

## UNIT-3 MPHYECC-5

### OP-AMP CIRCUITS

Submitted by:

Dr. Gargi Tiwari

Dept. of Physics

**Op-Amp-Applications:** A circuit is said to be linear, if there exists a linear relationship between its input and the output. Similarly, a circuit is said to be non-linear, if there exists a non-linear relationship between its input and output.

Op-amps can be used in both linear and non-linear applications. The following are the basic applications of op-amp –

Inverting Amplifier

Non-inverting Amplifier


Voltage follower

In this notes you will find these basic applications in detail.
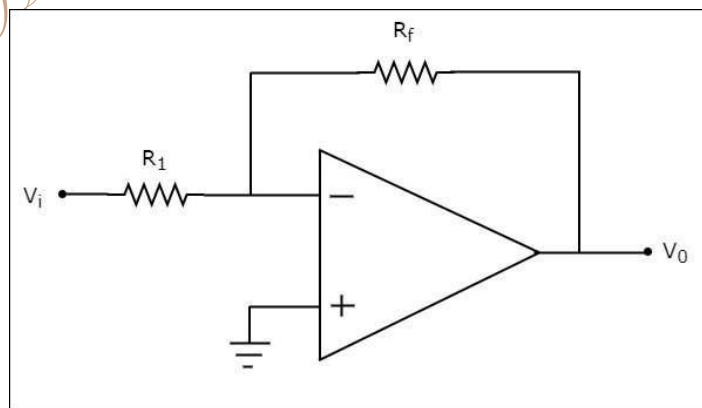
#### **Inverting Amplifier**

An inverting amplifier takes the input through its inverting terminal through a resistor  $R_1$ , and produces its amplified version as the output. This amplifier not only amplifies the input but also inverts it (changes its sign).

The **circuit diagram** of an inverting amplifier is shown in the following figure –



Note that for an op-amp, the voltage at the inverting input terminal is equal to the voltage at its non-inverting input terminal. Physically, there is no short between those two terminals but **virtually**, they are in **short** with each other. In the circuit shown above, the non-inverting input terminal is connected to ground. That means zero volts is applied at the non-inverting input terminal of the op-amp.

According to the **virtual short concept**, the voltage at the inverting input terminal of an op-amp will be zero volts.

The **nodal equation** at this terminal's node is as shown below

$$\begin{aligned} \frac{0 - V_i}{R_1} + \frac{0 - V_0}{R_f} &= 0 \\ \Rightarrow \frac{-V_i}{R_1} &= \frac{V_0}{R_f} \\ \Rightarrow V_0 &= \left(-\frac{R_f}{R_1}\right) V_i \\ \Rightarrow \frac{V_0}{V_i} &= \frac{-R_f}{R_1} \end{aligned}$$

The ratio of the output voltage  $V_0$  and the input voltage  $V_i$  is the voltage-gain or gain of the amplifier. Therefore, the **gain of inverting amplifier** is equal to  $\frac{-R_f}{R_1}$ .


Note that the gain of the inverting amplifier is having a **negative sign**. It indicates that there exists a **180° phase difference between the input and the output**.

### **Non-Inverting Amplifier**

A non-inverting amplifier takes the input through its non-inverting terminal, and produces its amplified version as the output. As the name suggests, this

amplifier just amplifies the input, without inverting or changing the sign of the output.

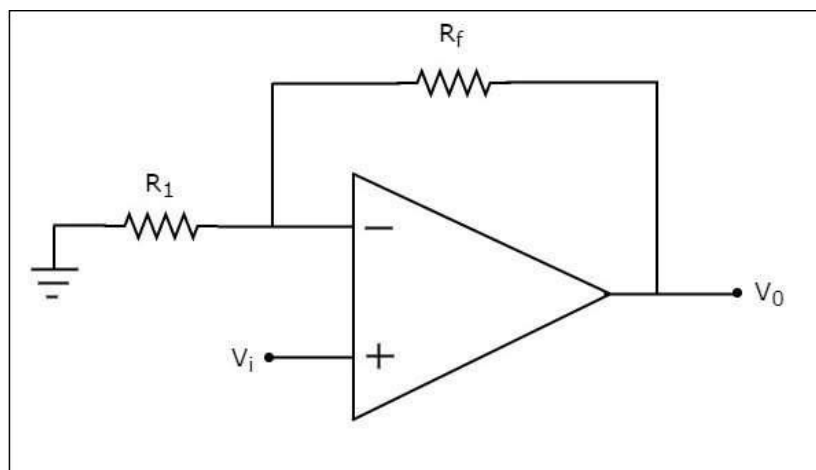The **circuit diagram** of a non-inverting amplifier is shown in the following figure –



In the above circuit, the input voltage  $V_i$  is directly applied to the non-inverting input terminal of op-amp. So, the voltage at the non-inverting input terminal of the op-amp will be  $V_i$ .

By using **voltage division principle**, we can calculate the voltage at the inverting input terminal of the op-amp as shown below –

$$\Rightarrow V_i = V_0 \left( \frac{R_1}{R_1 + R_f} \right)$$

According to the virtual short concept, the voltage at the inverting input terminal of an op-amp is same as that of the voltage at its non-inverting input terminal.

$$\Rightarrow V_0 \left( \frac{R_1}{R_1 + R_f} \right) = V_i$$

$$\Rightarrow \frac{V_0}{V_i} = \frac{R_1 + R_f}{R_1}$$

$$\Rightarrow \frac{V_0}{V_i} = 1 + \frac{R_f}{R_1}$$


Now, the ratio of output voltage  $V_0$  and input voltage  $V_i$  or the voltage-gain or gain of the non-inverting amplifier is equal to  $1 + \frac{R_f}{R_1}$

Note that the gain of the non-inverting amplifier is having a positive sign. It indicates that there is **no phase difference between the input and the output**.
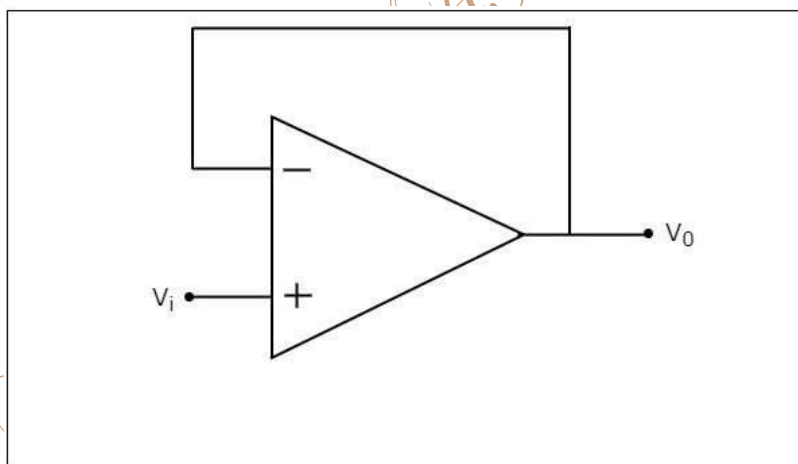
### **Voltage follower**

A voltage follower is an electronic circuit, which produces an output that follows the input voltage. It is a special case of non-inverting amplifier.

If we consider the value of feedback resistor,  $R_f$  as zero ohms and (or) the value of resistor,  $1$  as infinity ohms, then a non-inverting amplifier becomes a voltage follower. The circuit diagram of a voltage follower is shown in the following figure –



In the above circuit, the input voltage  $V_i$  is directly applied to the non-inverting input terminal of the op-amp. So, the voltage at the non-inverting input terminal of op-amp is equal to  $V_i$ . Here, the output is directly connected to the inverting input terminal of op-amp. Hence, the voltage at the inverting input terminal of op-amp is equal to  $V_0$ .

