

UNIT-3 MPHYCC-7

Submitted by:

Dr. Gargi Tiwari

Dept. of Physics

Differentiator and Integrator


The electronic circuits which perform the mathematical operations such as differentiation and integration are called as differentiator and integrator, respectively.

Here we will discuss in detail about op-amp based **differentiator** and integrator.

Note: These also come under linear applications of op-amp.

Differentiator

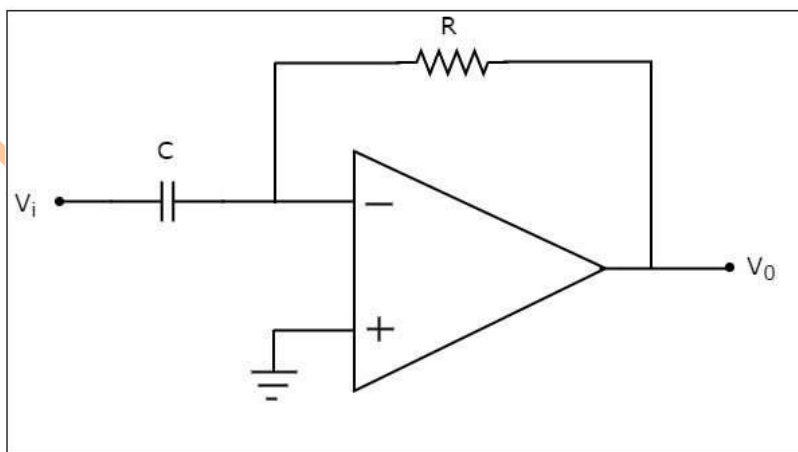A differentiator is an electronic circuit that produces an output equal to the first derivative of its input. An op-amp based differentiator produces an output, which is equal to the differential of input voltage that is applied to its inverting terminal. The circuit diagram of an op-amp based differentiator is shown in the following figure –



In the above circuit, the non-inverting input terminal of the op-amp is connected to ground. That means zero volts is applied to its non-inverting input terminal. According to the virtual short concept, the voltage at the inverting input terminal of op-amp will be equal to the voltage present at its non-inverting input terminal. So, the voltage at the inverting input terminal of op-amp will be zero volts. The nodal equation at the inverting input terminal's node is –

$$C \frac{d(0 - V_i)}{dt} + \frac{0 - V_0}{R} = 0$$

$$-C \frac{dV_i}{dt} = \frac{V_0}{R}$$

$$V_0 = -RC \frac{dV_i}{dt}$$


If $RC=1\text{sec}$, then the output voltage V_0 will be –

$$V_0 = -\frac{dV_i}{dt}$$

Thus, the op-amp based differentiator circuit shown above will produce an output, which is the differential of input voltage V_i , when the magnitudes of impedances of resistor and capacitor are reciprocal to each other. Note that the output voltage V_0 is having a **negative sign**, which indicates that there exists a 180° phase difference between the input and the output.

Integrator

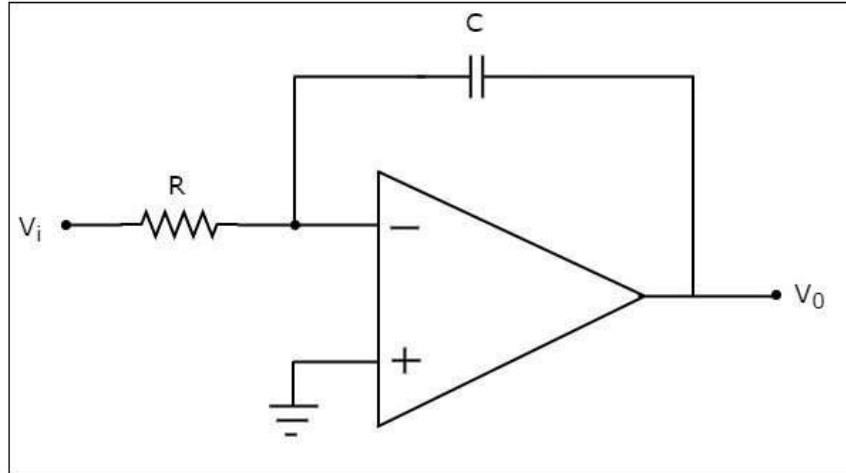An integrator is an electronic circuit that produces an output that is the integration of the applied input. This section discusses about the op-amp based integrator. An op-amp based integrator produces an output, which is an integral of the input voltage applied to its inverting terminal. The circuit diagram of an op-amp based integrator is shown in the following figure –



In the circuit shown above, the non-inverting input terminal of the op-amp is connected to ground. That means zero volts is applied to its non-inverting input terminal. According to virtual short concept, the voltage at the inverting input terminal of op-amp will be equal to the voltage present at its non-inverting input terminal. So, the voltage at the inverting input terminal of op-amp will be zero volts.

The nodal equation at the inverting input terminal is –

$$\frac{0-V_i}{R} + C \frac{d(0-V_0)}{dt} = 0$$

$$\frac{-V_i}{R} = C \frac{dV_0}{dt}$$

$$\frac{dV_0}{dt} = \frac{-V_i}{RC}$$

$$dV_0 = \left(\frac{-V_i}{RC} \right) dt$$

Integrating both sides of the equation shown above, we get –

$$\int dV_0 = \int \left(\frac{-V_i}{RC} \right) dt$$

$$V_0 = -\frac{1}{RC} \int V_i dt$$

If $RC=1\text{sec}$, then the output voltage, V_0 will be –

$$V_0 = - \int V_i dt$$

So, the op-amp based integrator circuit discussed above will produce an output, which is the integral of input voltage V_i , when the magnitude of impedances of resistor and capacitor are reciprocal to each other.

Note – The output voltage, V_0 is having a negative sign, which indicates that there exists 180° phase difference between the input and the output.