

Unijunction Transistor (UJT)


Amarendra Narayan

A Unijunction Transistor (UJT) is a three terminal semiconductor switching device. It consists of a bar of n-type silicon material with a terminal attached at its two ends known as base 1 and base 2. A third terminal is connected with a heavily doped p-type material alloyed into the bar part way along its length, and is known as the emitter. Since there is only one rectifying junction within the device, it is called a 'Unijunction' transistor. The unijunction transistor exhibits negative resistance in its characteristics. It finds use in relaxation oscillators in variety of applications.

Construction of Unijunction Transistor (UJT)

A Unijunction Transistor is constructed by forming a pn-junction between a lightly doped N type silicon bar and a heavily doped P type material on one side as shown in the figure. The ohmic contact on either ends of the silicon bar is termed as Base 1 (B1) and Base 2 (B2) and P-type terminal is named as emitter.

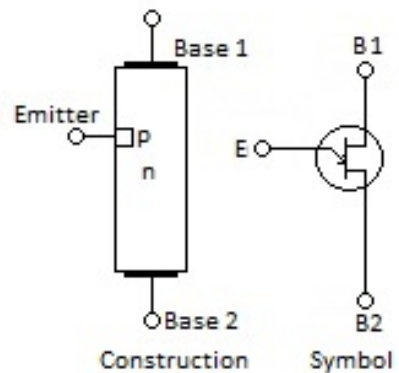The emitter junction is placed such that it is closer to Base 1 than to Base 2. The symbol of UJT is similar to that of JFET except that the emitter arrowhead for UJT is bent in the direction in which conventional current flows.




How does a Unijunction Transistor (UJT) work

The simplified equivalent circuit (at Figure 3 below) shows that N-type channel consists of two resistors R_{B2} and R_{B1} in series with an equivalent diode, D representing the PN junction. The emitter PN junction is fixed along the ohmic channel during its manufacturing process.

The variable resistance R_{B2} is provided between the terminals Emitter (E) and Base 2 (B1), the R_{B1} between the terminals Emitter (E) and Base 1 (B1). Since the PN junction is closer to B1, the value of R_{B1} will be less than the variable resistance R_{B2} .

A voltage divider network is formed by the series combination of resistances R_{B2} and R_{B1} . When a voltage is applied across the semiconductor device, the potential will be in proportion to the position of base points along the channel.

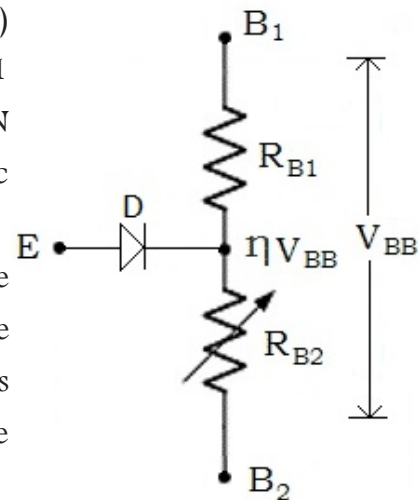The Emitter (E) acts as input when employed in a circuit, as the terminal B2 is grounded. The terminal B1 is positively biased with respect to B2 when a voltage (V_{BB}) applied across the terminals B1



and B2. When the emitter input is zero, the voltage across resistance RB2 of the voltage divider circuit is calculated by

$$V_{RB2} = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{BB}$$

The ‘intrinsic stand-off ratio’ (η) of the Unijunction Transistor is defined as the ratio of RB2 to RBB. Most UJT’s have η value ranging from 0.5 to 0.8. The PN junction is reverse biased if the voltage applied at the emitter is less than the sum of voltage developed across resistance RB2 (ηV_{BB}) and the voltage drop across a forward biased PN junction, V_f . i.e. $V_E < \eta V_{BB} + V_f$. A very high impedance is developed in this situation prompting device to move into non-conducting state i.e., it will be switched off and no current flows through it. The UJT begins to conduct when the PN junction is forward biased. This is achieved when voltage applied to the emitter terminal, $V_E > V_{RB1} + V_f$, i.e. $V_E > \eta V_{BB} + V_f$. This results in larger flow of emitter current from emitter region to base region. Increase in emitter current results in injection of large number of conduction electrons in the region between emitter and Base 2. This reduces the resistance between emitter and Base 2, resulting in a reduction in total resistance between Base 1 and base 2. As a result a large current flows between base 1 and base 2.

The Unijunction Transistor (UJT) will act as voltage breakdown device, when the input applied between emitter and base 1 reduces below breakdown value i.e., R_{B1} increases to a higher value. This shows that R_{B1} depends on the emitter current and it is variable.

Characteristics Curve of Unijunction Transistor (UJT)

The characteristics of Unijunction Transistor (UJT) is given below. The figure shows Emitter current I_E on the x-axis and V_E on the y-axis. The curve has three regions: (1) Cutoff region (2) Negative Resistance region, (3) Saturation region.

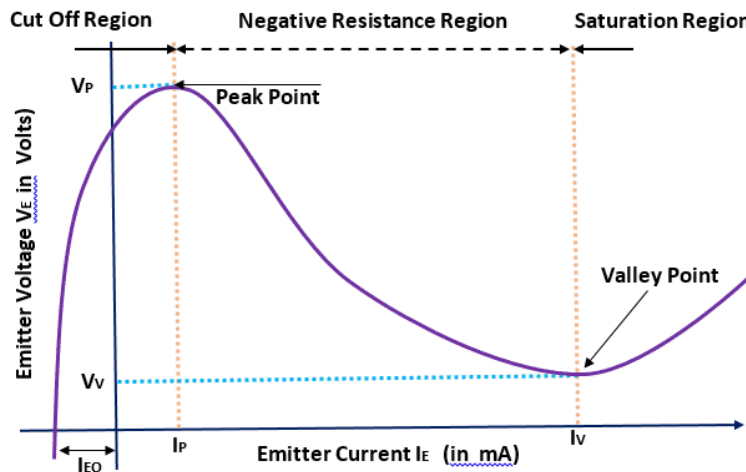


Fig. 4 – Characteristics of Unijunction Transistor (UJT)

Cutoff region

Cutoff region is the area where the Unijunction Transistor (UJT) doesn't get sufficient voltage to turn on. The applied voltage V_E hasn't reached the triggering point, thus making transistor to remain in off state.

Negative Resistance region

When the emitter reaches the triggering voltage, V_{TRIG} , Unijunction Transistor (UJT) will turn on. After a certain time, if the voltage applied to the emitter lead increases, it will reach out at V_{PEAK} . The voltage drops from V_{PEAK} to Valley Point even though the current increases (negative resistance).

Saturation

Saturation region is the part of characteristic curve in which the current and voltage both increase, if the applied voltage to emitter terminal increases.


Applications of Unijunction Transistor (UJT)

The Unijunction Transistor can be employed in variety of applications such as.

- Switching Device
- Triggering Device for Triacs and SCR's
- Timing Circuits
- For phase control
- In sawtooth generators
- In simple relaxation oscillators

Application of Unijunction Transistor (UJT) in Relaxation Oscillator

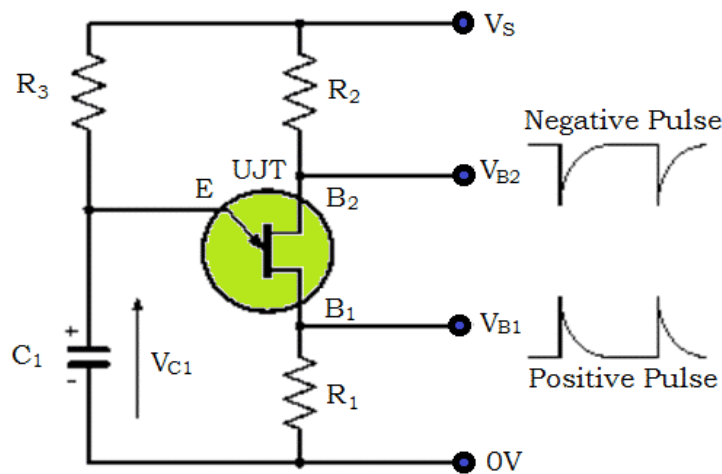UJT Relaxation Oscillator can be practically viewed by the following circuit.



Use of Unijunction Transistor (UJT) in Relaxation Oscillator

A relaxation oscillator is a circuit that generates a sawtooth waveform. A typical circuit is shown above. The capacitor C_1 is charged through the resistor R_3 until V_E reaches the peak point. (The UJT's emitter terminal has no effect on C_1 until peak point is reached). When the emitter voltage reaches peak voltage point, the emitter-base 1 resistance diminishes which results in rapid discharge of the capacitor C_1 . The capacitor C_1 discharges until V_E goes below the valley point. The emitter-base 1 resistance will then return back to high resistance state, thus completing the cycle. The capacitor C_1 is now free to charge again.

Application of Unijunction Transistor (UJT) in Speed Control Circuit

Speed Control Circuit is one of the typical applications of UJT to produce a set of pulses to trigger and control Thyristor. We can adjust the speed of universal motors by using UJT as a triggering circuit in combination with SCR and Triacs.

Advantages of Unijunction Transistor (UJT)

The advantages of Unijunction Transistor include:

- low cost
- negative resistance characteristics
- Requires low value of triggering current
- A stable triggering voltage
- Low power absorbing device

Disadvantage of Unijunction Transistor (UJT)

The main disadvantage of Unijunction Transistor is its inability to provide appropriate amplification.

Further reading: <https://electricalfundablog.com/unijunction-transistor-ujt-construction-working-characteristics-curve-applications/>

Also see <https://electricalfundablog.com/thyristor-working-vi-characteristics/>

<https://www.elprocus.com/introduction-to-uni-junction-transistor-construction-and-operation/>